

DIGITAL SYSTEM DESIGN LAB CSE-308L

SEMESTER:6TH



LAB REPORT # 2

Submitted By: Zainab Khalid
Registration No:19PWCSE1743
Section: A
Submitted to: Mam Madeeha Sher

DEPARTMENT OF COMPUTER SYSTEMS ENGINEERING
UNIVERSITY OF ENGINEERING AND TECHNOLOGY PESHAWAR

LAB No 2

INTRODUCTION TO MODELSIM AND GATE LEVEL MODELING

Objectives:

This lab will enable students to:

- Learn top down and bottom up design methodologies
- Data flow level modeling
- Data gate level modeling

Data Gate Level Modeling.

Designing circuits using basic logic gates is known as gate-level modeling. A digital circuit is implemented using logic gates and interconnections between these gates.

Data Flow Level Modeling.

Dataflow modeling uses a number of operators that act on operands to produce the desired results. Verilog HDL provides about 30 operator types like &, |, ^, ==, >, <, ? etc. Dataflow modeling uses continuous assignments and the keyword *assign*. It is called continuous assignment because it remains active all the time.

assign out = a&b;

The left hand side variable must be of type wire. At the right hand side, there can be a single variable or expression and of type reg or wire.

Operators used:

Arithmetic: +, -, *, /

Logical: &&, ||

Bitwise: &, |, ~, ^

Reduction: ~|, ~&, ~^

Shift: <<, >>

Equality: ==, !=, (case equality: ===, !==)

Conditional: ?, :

Concatenation: {}

Example: a=01;b=110; c={a,b};

Replication: {{}}

Example: A=111111000000

x={6{1}}; y={6{0}};


A={x,y} or A={6{1},6{0}};

TASK 1:

4 bit Ripple Carry Adder

Block Diagram:

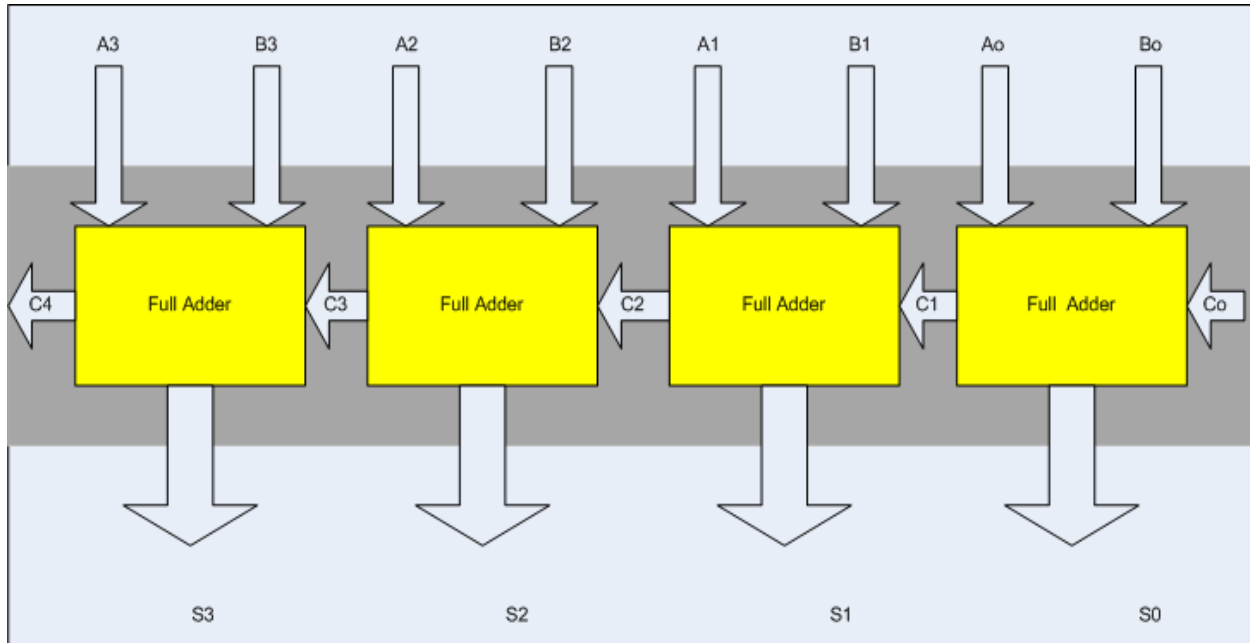Following is the block diagram of a 4 bit Ripple Carry Adder.



I/O Connection:

Ground “Co” Permanently and connect S0-S3 with four LEDs also connect C4 to another LED.

Steps for task 1a:

The following steps should be performed while designing a 4 bit RCA adder

ModelSim:

- 1- First implement a Full adder using data gate level modeling.

Data Gate Level Modeling.

Code (Full Adder):

```

1 //Structural Model : Half Adder
2 module half_adder(output S,C,input A,B);
3   xor(S,A,B);
4   and(C,A,B);
5 endmodule
6
7 //Structural Model : Full Adder
8 module full_adder(S,Cout,A,B,Cin);
9   input A,B,Cin;
10  output S,Cout;
11  wire s1,c1,c2;
12  half_adder HA1(s1,c1,A,B);
13  half_adder HA2(S,c2,s1,Cin);
14  or ol(Cout,c1,c2);
15 endmodule
16

```

2- Simulate the Full adder with a test bench.

Code (Test Bench For Full Adder):

```

17 module test_FA(); //test bench to test FA (Full Adder)
18   // Inputs are regs here
19   reg A, B, Cin;
20   // Outputs are wires here
21   wire S, Cout;
22   // Instantiate the Unit/Design Under Test (U/DUT)
23   // FA dut (S, Cout, A, B, Cin); // Positional association
24   full_adder fa(.A(A), .B(B), .Cin(Cin), .S(S), .Cout(Cout)); // Explicit association
25
26   initial begin
27     // Initialize Inputs
28     A = 0; B = 0; Cin = 0;
29     #10
30     Cin = 1;
31     #10
32     B = 1;
33     #10
34     A = 1;
35     #10
36     A = 0;
37     #10
38     Cin = 0;
39   end
40
41   initial begin
42     $monitor("A=%b,B=%b,Cin=%b-->Sum=%b,Cout=%b \n",A,B,Cin,S,Cout);
43   end
44
45 endmodule

```

Output (Full Adder):

```

# Compile of fulladder.v was successful.
vsim work.test_FA
# vsim work.test_FA
# Loading work.test_FA
# Loading work.full_adder
# Loading work.half_adder
run
# A=0,B=0,Cin=0-->Sum=0,Cout=0
#
# A=0,B=0,Cin=1-->Sum=1,Cout=0
#
# A=0,B=1,Cin=1-->Sum=0,Cout=1
#
# A=1,B=1,Cin=1-->Sum=1,Cout=1
#
# A=0,B=1,Cin=1-->Sum=0,Cout=1
#
# A=0,B=1,Cin=0-->Sum=1,Cout=0
#

```

3- Instantiate the Full adder four times and connect the circuit as shown.

Code (Ripple Adder):

```

17 //Structural Model : 4 Bit Ripple Carry Adder
18 module ripple_adder_4bit (Cout, Sum, A, B, Cin) ;
19     output [3:0] Sum;
20     output Cout;
21     input [3:0] A, B;
22     input Cin;
23     wire c1, c2, c3;
24     //full_adder fa (S, Cout, A, B, Cin) ;
25     full_adder FA1 (Sum[0], c1, A[0], B[0], Cin),
26     FA2 (Sum[1], c2, A[1], B[1], c1),
27     FA3 (Sum[2], c3, A[2], B[2], c2),
28     FA4 (Sum[3], Cout, A[3], B[3], c3) ;
29 endmodule

```

4- Now again write a test bench and simulate the 4 bit RCA.

Code (Test Bench For Ripple Adder):

```

31 //Test Bench : 4 Bit Ripple Carry Adder
32 module test_ripple_adder_4bit();
33 // Inputs
34 reg [3:0] A;
35 reg [3:0] B;
36 reg Cin;
37 // Outputs
38 wire [3:0] Sum;
39 wire Cout;
40 // Instantiate the Unit Under Test (UUT)
41 ripple_adder_4bit rpa(.Sum(Sum), .Cout(Cout), .A(A), .B(B), .Cin(Cin));
42 initial
43     begin
44
45         $monitor("A=%d   B=%d   Cin=%d   Sum=%d           Cout=%d",A,B,Cin,Sum,Cout);
46         A=4'b0000;B=4'b0000;Cin=1'b0;
47         #10
48         A=4'b0010;B=4'b0010;Cin=1'b0;
49         #10
50         A=4'b0010;B=4'b0100;Cin=1'b0;
51         #10
52         A=4'b0110;B=4'b1010; Cin=1'b0;
53         #10
54         A=4'b1111;B=4'b1111;Cin=1'b0;
55     end
56 endmodule

```

Output (Ripple Adder):

```

# Compile of example.v was successful.
vsim work.test_ripple_adder_4bit
# vsim work.test_ripple_adder_4bit
# Loading work.test_ripple_adder_4bit
# Loading work.ripple_adder_4bit
# Loading work.full_adder
# Loading work.half_adder
run
# A= 0   B= 0 Cin=0 Sum= 0 Cout=0
# A= 2   B= 2 Cin=0 Sum= 4 Cout=0
# A= 2   B= 4 Cin=0 Sum= 6 Cout=0
# A= 6   B=10 Cin=0 Sum= 0 Cout=1
# A=15   B=15 Cin=0 Sum=14 Cout=1

```

Xilinx:

1. Make new project in Xilinx and add the files that you simulated in ModelSim.
2. Add User Constraint File inputs should be locked with the switches, C0 should be permanently "0" while S0-S4 and C4 with LEDS

Task 1b:

Design the 4 bit full adder using data flow level modeling.

Data Flow Level Modeling:

Code (Ripple Adder):

◆	ln #	
	1	module SUM (S, A, B, Cin);
	2	output S;
	3	input A, B, Cin;
	4	// Behavioral Code
	5	assign S = A^B^Cin;
	6	
	7	endmodule
	8	
	9	module CARRY (Cout, A, B, Cin);
	10	output Cout;
	11	input A, B, Cin;
	12	// Behavioral Code
	13	assign Cout = (A&B) (B&Cin) (A&Cin);
	14	endmodule
	15	
	16	module FAl (Sum, Cout, A, B, Cin);
	17	output Sum, Cout;
	18	input A, B, Cin;
	19	// Structural Code
	20	SUM s1 (.S(Sum), .A(A), .B(B), .Cin(Cin));
	21	CARRY c1 (.Cout(Cout), .A(A), .B(B), .Cin(Cin));
	22	endmodule
	23	
	24	module RCA (Cout, S, A, B, Cin);
	25	output Cout;
	26	output [3:0] S;
	27	input [3:0] A, B;
	28	input Cin;
	29	wire [2:0] C; //Intermediate/Internal Carries
	30	// FAl ; //FAl's Interface (I/O Pins)
	31	FAl fa0 (S[0], C[0], A[0], B[0], Cin);
	32	FAl fa1 (S[1], C[1], A[1], B[1], C[0]);
	33	FAl fa2 (S[2], C[2], A[2], B[2], C[1]);
	34	FAl fa3 (S[3], Cout, A[3], B[3], C[2]);
	35	endmodule
	36	

Code (Test Bench):

```

37 module stim_RCA(); //test bench
38 reg [3:0]A,B; //4 bits inputs
39 reg Cin;
40 wire Cout; //1 bits output
41 wire [3:0]S; //4 bits outputs
42 RCA r(Cout, S, A, B,Cin);
43 initial
44     begin
45         $monitor("A=%d B=%d Cin=%d Sum=%d Cout=%d",A,B,Cin,S,Cout);
46         A=4'b0000;B=4'b0000;Cin=1'b0;
47         #10
48         A=4'b0010;B=4'b0010;Cin=1'b0;
49         #10
50         A=4'b0010;B=4'b0100;Cin=1'b0;
51         #10
52         A=4'b0110;B=4'b1010; Cin=1'b0;
53         #10
54         A=4'b1111;B=4'b1111;Cin=1'b0;
55     end
56 endmodule

```

Output:

```

# Compile of rippleadder.v was successful.
vsim work.stim_RCA
# vsim work.stim_RCA
# Loading work.stim_RCA
# Loading work.RCA
# Loading work.FA1
# Loading work.SUM
# Loading work.CARRY
run
#A=0 B=0 Cin=0 Sum=0 Cout=0
#A=2 B=2 Cin=0 Sum=4 Cout=0
#A=2 B=4 Cin=0 Sum=6 Cout=0
#A=6 B=10 Cin=0 Sum=0 Cout=1
#A=15 B=15 Cin=0 Sum=14 Cout=1

```

2nd Code:

```

1 module rippleadder(cout,sum,a,b,cin);
2 input cin; //1 bits input
3 input [3:0]a,b; //4 bits inputs
4 output cout; //1 bits output
5 output [3:0]sum; //4 bits outputs
6 assign {cout,sum}=a+b+cin; //behavioral modeling
7 endmodule
8
9 module stim_ripple(); //test bench
10 reg cin; //1 bits input
11 reg [3:0]a,b; //4 bits inputs
12 wire cout; //1 bits output
13 wire [3:0]sum; //4 bits outputs
14 rippleadder ra(cout,sum,a,b,cin);
15 initial
16     begin

```



```

16     begin
17     $display("A      B      Cin      Sum      Cout");
18     a=4;b=6;cin=1'b0;
19     #10
20     $display("%d %d %d      %d      %d",a,b,cin,sum,cout);
21     a=11;b=5;cin=1'b0;
22     #10
23     $display("%d %d %d      %d      %d",a,b,cin,sum,cout);
24     a=9;b=3;cin=1'b0;
25     #10
26     $display("%d %d %d      %d      %d",a,b,cin,sum,cout);
27     a=2;b=1;cin=1'b0;
28     #10
29     $display("%d %d %d      %d      %d",a,b,cin,sum,cout);
30     a=5;b=3;cin=1'b0;
31     #10
32     $display("%d %d %d      %d      %d",a,b,cin,sum,cout);
33     end
34
35 //initial
36     //begin
37     //$monitor("A=%b  B=%b      Cin=%b      Sum=%b      Cout=%b",a,b,cin,sum,cout);
38     //end
39 endmodule

```

Output:

```

# Compile of 4bitrippleadder.v was successful.
vsim work.stim_ripple
# vsim work.stim_ripple
# Loading work.stim_ripple
# Loading work.rippleadder
run
# A B Cin Sum Cout
# 4 6 0 10 0
# 11 5 0 0 1
# 9 3 0 12 0
# 2 1 0 3 0
# 5 3 0 8 0

```