

DIGITAL SYSTEM DESIGN LAB CSE-308L

SEMESTER:6TH



LAB REPORT # 7

Submitted By: Zainab Khalid
Registration No:19PWCSE1743

Section: A

Submitted to: Mam Madeeha Sher

DEPARTMENT OF COMPUTER SYSTEMS ENGINEERING
UNIVERSITY OF ENGINEERING AND TECHNOLOGY PESHAWAR

LAB NO 7

DESIGN OF A LIGHT SWITCH



Objective:

Build a light switch controller such that when the push button is pressed the light if “off” turns “on” and if “on” turns “off”.


Block Diagram:

The top level block diagram is shown in the following figure. The second diagram is a more detailed view of the top level diagram. Synchronizer circuit is used to avoid the metastability problem which arises when synchronous digital system are fed with an asynchronous input. The level to pulse converter is there to convert level input from a push button into a pulse that is high for only one clock cycle. The switch button FSM is actually implementing the state machine for the requirement i-e when the push button is pressed the light if “off” turns “on” and if “on” turns “off”.

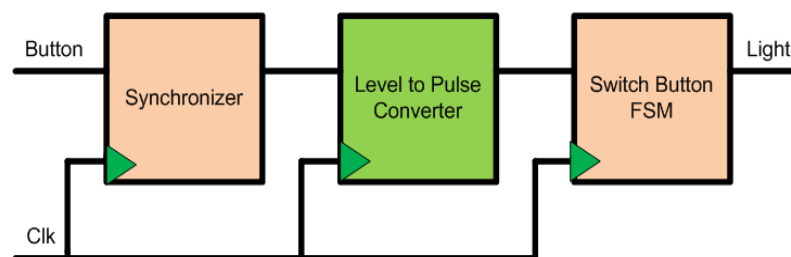 
I/O connection: Connect the button input to a push button on the S3BOARD and light output to LED.




Synchronizer Circuit:

 

Level to Pulse FSM:

 

Switch Button FSM:

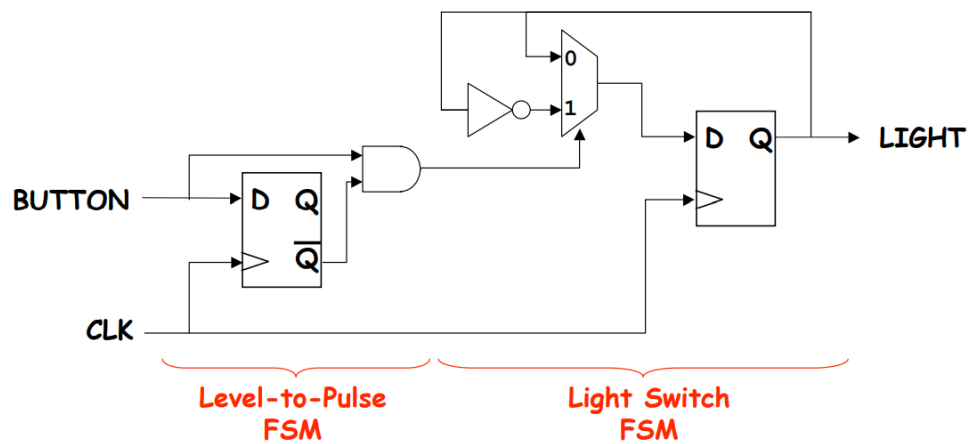

CODE:

```
module task2(clk,rst,in,out,pulse);

input clk,rst,in;
output out,pulse;
wire synin, CLK_1hz;

CLOCK_Divider CD1(clk,rst,CLK_1hz);
synchron ss2(in,CLK_1hz,rst,synin);
task1 t1(clk,rst,synin,pulse);

parameter s0=0;
parameter s1=1;
reg state, next_state,out;

always @(posedge CLK_1hz)
begin
    if(~rst)
        begin
            state=s0;
        end
    else
        state=next_state;
end
always @(*)
begin
    case(state)
        s0:
            begin
                if(pulse==0)
                    begin
                        next_state=s0;
                        out=0;
                    end
                else
                    begin
                        next_state=s1;
                        out=1;
                    end
            end
        s1:
            begin
                if(pulse==1)
                    begin
                        next_state=s0;
                        out=0;
                    end
                else
                    begin
                        next_state=s1;
                    end
            end
    endcase
end
end
```

```

                                out=1;
                                end
                                end
                                endcase
                                end
                                endmodule

//designing the pulse generator
module task1(clk,rst,in,out);
input clk, rst,in;
output out;
wire synin, CLK_1hz;

CLOCK_Divider CD(clk,rst,CLK_1hz);
synchron ssl(in,CLK_1hz,rst,synin);

parameter s0=0;
parameter s1=1;
reg state, next_state,out;

always @(posedge CLK_1hz)
begin
    if(~rst)
    begin
        state=s0;
    end

    else
        state=next_state;
end
always @(*)
begin
    case(state)
        s0:
        begin
            if(synin==0)
            begin
                next_state=s0;
                out=0;
            end

            else
            begin
                next_state=s1;
                out=1;
            end

        end
        s1:
        begin
            if(synin==1)
            begin
                next_state=s1;
                out=0;
            end
        end
    endcase
end

```

```

        end
        else
        begin
            next_state=s0;
            out=0;
        end
    end
endcase
end
endmodule
//designing the synchronizer
module synchron(in, clk, rst,synin);

input in,clk,rst;
output synin;

wire out;

D_FF ff1(out,in,clk,rst);
D_FF ff2(synin,out,clk,rst);

endmodule
//designing the D flipflop
module D_FF (q, d, clock, reset);

    output q;
    input d, clock, reset;

    reg q;

    always @(posedge clock)
    begin
        if (~reset)
            q = 1'b0;
        else
            q = d;
        end
    end

endmodule
//designing the clock divider
module CLOCK_Divider(input CLK_100MHz,input RESET,output reg CLK_1hz);

    integer c=0;
    always @(posedge CLK_100MHz)
    begin
        if(~RESET)
        begin
            c = 0;
            CLK_1hz=1;
        end
        else

```

```

begin
    c = c+1;
    if(c==1000000)
    begin
        CLK_1hz = ~CLK_1hz;
        c=0;
    end
end
end
endmodule

```

OUTPUT:

